



## **CSE 112: Computer Organization and Architecture**

### **Major Task Report**

#### **Made By:**

Ahmed Wael Samir Abdelmegied 20P7271 (Group Leader)

Ahmed Hossam Moussa Sakr 20P1009

Tamer Ihab Mohamed Abdelwahab 20P5567

Omar Ahmed Mohamed Gamaleldin Swelam 21P0405

Mohamed Tarek Mohamed Abdalla Ahmed Khafagy 20P6211

# Phase 1

## The MIPS Register Description

In order to implement the MIPS Register File, we needed to implement a normal register module, a 5-32 decoder and a 32x1 multiplexer, all to be used as components to implement the main module required “RegisterFile”. Firstly, we implemented a normal register in a module called “RegDef”.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity RegDef is
6
7      Port ( input : in  STD_LOGIC_VECTOR (31 downto 0) ;
8            rst : in  STD_LOGIC ;
9            clk : in  STD_LOGIC;
10           load : in  STD_LOGIC;
11           increment : in STD_LOGIC;
12           output : out STD_LOGIC_VECTOR (31 downto 0) );
13 end RegDef;
14
15 architecture Behavioral of RegDef is
16     signal temporary : std_logic_vector (31 downto 0) :=x"00000000";
17     begin
18
19         process (clk, rst)
20             begin
21                 if (rst = '1') then
22                     temporary <= (others => '0');
23                 elsif (FALLING_EDGE(clk) and load = '1') then
24                     temporary <= input;
25                 elsif (FALLING_EDGE(clk) and increment = '1') then
26                     temporary <= STD_LOGIC_VECTOR(signed(temporary) + 1);
27
28                 end if;
29             end process;
30
31             output <= temporary;
32
33     end Behavioral;
```

The “RegDef” register is the regular implementation of a register that takes the following inputs: The data input to the register, a reset, a clock, load and increment. It produces only one output. In case the reset = ‘1’, the output is filled with zeros. However, when the reset is equal to ‘0’ and there is a clock pulse received, at the falling edge of the clock, if the load = ‘1’, the input value to the register is loaded and transferred to the output, however, if the increment = ‘1’, the output is incremented by 1.

Next, we implemented the 5-32 decoder called “The Decoder”. Its entity contains two input ports which are called “input” and “enable”, and one output port called “output”. The decoder job will be taking 5-bit input and converting it to 32-bit output, this will be used in writing data to a register, where the 5-bits will be the address of the register for the data to be written in, and the 32-output will be connected to 32 registers of the MIPS Register File as enable lines, whichever one is activated during the writing process, the equivalent register will be selected and the data will be written to it.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity TheDecoder is
5      Port (
6          input : in STD_LOGIC_VECTOR (4 downto 0);
7          enable : in STD_LOGIC;
8          output : out STD_LOGIC_VECTOR (31 downto 0));
9  end TheDecoder;
10
11  architecture Behavioral of TheDecoder is
12
13  begin
14
15  output <= (others => 'Z') when enable = '0' else
16      "00000000000000000000000000000001" when input = "00000" else
17      "00000000000000000000000000000010" when input = "00001" else
18      "000000000000000000000000000000100" when input = "00010" else
19      "0000000000000000000000000000001000" when input = "00011" else
20      "0000000000000000000000000000010000" when input = "00100" else
21      "00000000000000000000000000000100000" when input = "00101" else
22      "000000000000000000000000000001000000" when input = "00110" else
23      "0000000000000000000000000000010000000" when input = "00111" else
24      "0000000000000000000000000000100000000" when input = "01000" else
25      "00000000000000000000000000001000000000" when input = "01001" else
26      "000000000000000000000000000010000000000" when input = "01010" else
27      "0000000000000000000000000000100000000000" when input = "01011" else
28      "0000000000000000000000000000100000000000" when input = "01100" else
29      "0000000000000000000000000000100000000000" when input = "01101" else
30      "0000000000000000000000000000100000000000" when input = "01110" else
31      "0000000000000000000000000000100000000000" when input = "01111" else
32      "0000000000000000000000000000100000000000" when input = "10000" else
33      "0000000000000000000000000000100000000000" when input = "10001" else
34      "0000000000000000000000000000100000000000" when input = "10010" else
35      "0000000000000000000000000000100000000000" when input = "10011" else
36      "0000000000000000000000000000100000000000" when input = "10100" else
37      "0000000000000000000000000000100000000000" when input = "10101" else
38      "0000000000000000000000000000100000000000" when input = "10110" else
39      "0000000000000000000000000000100000000000" when input = "10111" else
40      "00000000100000000000000000000000000000" when input = "11000" else
41      "00000001000000000000000000000000000000" when input = "11001" else
42      "00000010000000000000000000000000000000" when input = "11010" else
43      "00001000000000000000000000000000000000" when input = "11011" else
44      "00010000000000000000000000000000000000" when input = "11100" else
45      "00100000000000000000000000000000000000" when input = "11101" else
46      "01000000000000000000000000000000000000" when input = "11110" else
47      "10000000000000000000000000000000000000" when input = "11111" else
48      (others => 'X');
49
50  end Behavioral;
51

```

Last but not least, we implemented a 32x1 multiplexer, which takes 32 inputs which will be the data stored in the 32 registers and produces only one output which will be the data required to be read from the selected register.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Mux32x1 is
5      Port ( S : in  STD_LOGIC_VECTOR (4 downto 0);
6            i0 : in  STD_LOGIC_VECTOR (31 downto 0);
7            i1 : in  STD_LOGIC_VECTOR (31 downto 0);
8            i2 : in  STD_LOGIC_VECTOR (31 downto 0);
9            i3 : in  STD_LOGIC_VECTOR (31 downto 0);
10           i4 : in  STD_LOGIC_VECTOR (31 downto 0);
11           i5 : in  STD_LOGIC_VECTOR (31 downto 0);
12           i6 : in  STD_LOGIC_VECTOR (31 downto 0);
13           i7 : in  STD_LOGIC_VECTOR (31 downto 0);
14           i8 : in  STD_LOGIC_VECTOR (31 downto 0);
15           i9 : in  STD_LOGIC_VECTOR (31 downto 0);
16           i10: in  STD_LOGIC_VECTOR (31 downto 0);
17           i11: in  STD_LOGIC_VECTOR (31 downto 0);
18           i12: in  STD_LOGIC_VECTOR (31 downto 0);
19           i13: in  STD_LOGIC_VECTOR (31 downto 0);
20           i14: in  STD_LOGIC_VECTOR (31 downto 0);
21           i15: in  STD_LOGIC_VECTOR (31 downto 0);
22           i16: in  STD_LOGIC_VECTOR (31 downto 0);
23           i17: in  STD_LOGIC_VECTOR (31 downto 0);
24           i18: in  STD_LOGIC_VECTOR (31 downto 0);
25           i19: in  STD_LOGIC_VECTOR (31 downto 0);
26           i20: in  STD_LOGIC_VECTOR (31 downto 0);
27           i21: in  STD_LOGIC_VECTOR (31 downto 0);
28           i22: in  STD_LOGIC_VECTOR (31 downto 0);
29           i23: in  STD_LOGIC_VECTOR (31 downto 0);
30           i24: in  STD_LOGIC_VECTOR (31 downto 0);
31           i25: in  STD_LOGIC_VECTOR (31 downto 0);
32           i26: in  STD_LOGIC_VECTOR (31 downto 0);
33           i27: in  STD_LOGIC_VECTOR (31 downto 0);
34           i28: in  STD_LOGIC_VECTOR (31 downto 0);
35           i29: in  STD_LOGIC_VECTOR (31 downto 0);
36           i30: in  STD_LOGIC_VECTOR (31 downto 0);
37           i31: in  STD_LOGIC_VECTOR (31 downto 0);
38           output : out  STD_LOGIC_VECTOR (31 downto 0));
39  end Mux32x1;
```

```

40
41 architecture Behavioral of Mux32x1 is
42
43 begin
44
45     output <= i0  when S = "00000" else
46                i1  when S = "00001" else
47                i2  when S = "00010" else
48                i3  when S = "00011" else
49                i4  when S = "00100" else
50                i5  when S = "00101" else
51                i6  when S = "00110" else
52                i7  when S = "00111" else
53                i8  when S = "01000" else
54                i9  when S = "01001" else
55                i10 when S = "01010" else
56                i11 when S = "01011" else
57                i12 when S = "01100" else
58                i13 when S = "01101" else
59                i14 when S = "01110" else
60                i15 when S = "01111" else
61                i16 when S = "10000" else
62                i17 when S = "10001" else
63                i18 when S = "10010" else
64                i19 when S = "10011" else
65                i20 when S = "10100" else
66                i21 when S = "10101" else
67                i22 when S = "10110" else
68                i23 when S = "10111" else
69                i24 when S = "11000" else
70                i25 when S = "11001" else
71                i26 when S = "11010" else
72                i27 when S = "11011" else
73                i28 when S = "11100" else
74                i29 when S = "11101" else
75                i30 when S = "11110" else
76                i31 when S = "11111" else
77                (others => '2');
78
79 end Behavioral;
80

```

Consequently, we placed all the previous modules in a package called “RegPackage” to be used in implementing the main module “RegisterFile”.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use work.RegPackage.all;
4
5  entity RegisterFile is
6      Port ( read_sel1 : in  STD_LOGIC_VECTOR (4 downto 0);
7            read_sel2 : in  STD_LOGIC_VECTOR (4 downto 0);
8            write_sel  : in  STD_LOGIC_VECTOR (4 downto 0);
9            write_ena  : in  STD_LOGIC;
10           clk        : in  STD_LOGIC;
11           write_data : in  STD_LOGIC_VECTOR (31 downto 0);
12           data1      : out STD_LOGIC_VECTOR (31 downto 0);
13           data2      : out STD_LOGIC_VECTOR (31 downto 0));
14  end RegisterFile;

```

At the beginning, we included the previously created package “RegPackage” and declared the ports of the “RegisterFile” as described in the major task pdf.

Secondly, we declared a signal called ‘L’ with size of 32 bits to be used as the load enables of each register starting from L(0) to L(31) to select the required register in the writing process. Also, we declared 32 signals starting from “out0” till “out31” in order to hold the output of each register of the 32 registers to be used later on as the inputs of the 32x1 multiplexer to choose the required output in the reading process.

```

17
18  signal L, out0, out1, out2, out3, out4, out5, out6, out7, out8, out9, out10,
, out10, out11, out12, out13, out14, out15, out16, out17, out18, out19, out20, out21, out22,
, out22, out23, out24, out25, out26, out27, out28, out29, out30, out31: STD_LOGIC_VECTOR (31 downto 0);

```



Moreover, then we created onedecoder calling “TheDecoder” previous implementation, mapping the write\_sel to the input, the write\_ena to the enable and Signal ‘L’ to the output of the decoder.

```
22      onedecoder : TheDecoder port map (write_sel,write_ena,L);
```

After that, we created 32 Registers using the “RegDef” module and mapped the write\_data to the input of the registers except for “Reg0” to have 32 zeros to the input because it will represent \$zero, then, ‘0’ to the reset, clk to the clk, ‘L’ signal starting from L(0) to L(31) respectively to the load, ‘0’ to the increment, and from out0 to out31 respectively to the outputs of the registers.

```
23
24      Reg0      : RegDef      port map (x"00000000",'0',clk,L(0),'0',out0 ); --$zero
25      Reg1      : RegDef      port map (write_data,'0',clk,L(1),'0', out1 ); --$at
26      Reg2      : RegDef      port map (write_data,'0',clk,L(2),'0', out2 ); --$v0
27      Reg3      : RegDef      port map (write_data,'0',clk,L(3),'0', out3 ); --$v1
28      Reg4      : RegDef      port map (write_data,'0',clk,L(4),'0', out4 ); --$a0
29      Reg5      : RegDef      port map (write_data,'0',clk,L(5),'0', out5 ); --$a1
30      Reg6      : RegDef      port map (write_data,'0',clk,L(6),'0', out6 ); --$a2
31      Reg7      : RegDef      port map (write_data,'0',clk,L(7),'0', out7 ); --$a3
32      Reg8      : RegDef      port map (write_data,'0',clk,L(8),'0', out8 ); --$t0
33      Reg9      : RegDef      port map (write_data,'0',clk,L(9),'0', out9 ); --$t1
34      Reg10     : RegDef      port map (write_data,'0',clk,L(10),'0',out10 ); --$t2
35      Reg11     : RegDef      port map (write_data,'0',clk,L(11),'0',out11 ); --$t3
36      Reg12     : RegDef      port map (write_data,'0',clk,L(12),'0',out12 ); --$t4
37      Reg13     : RegDef      port map (write_data,'0',clk,L(13),'0',out13 ); --$t5
38      Reg14     : RegDef      port map (write_data,'0',clk,L(14),'0',out14 ); --$t6
39      Reg15     : RegDef      port map (write_data,'0',clk,L(15),'0',out15 ); --$t7
40      Reg16     : RegDef      port map (write_data,'0',clk,L(16),'0',out16 ); --$s0
41      Reg17     : RegDef      port map (write_data,'0',clk,L(17),'0',out17 ); --$s1
42      Reg18     : RegDef      port map (write_data,'0',clk,L(18),'0',out18 ); --$s2
43      Reg19     : RegDef      port map (write_data,'0',clk,L(19),'0',out19 ); --$s3
44      Reg20     : RegDef      port map (write_data,'0',clk,L(20),'0',out20 ); --$s4
45      Reg21     : RegDef      port map (write_data,'0',clk,L(21),'0',out21 ); --$s5
46      Reg22     : RegDef      port map (write_data,'0',clk,L(22),'0',out22 ); --$s6
47      Reg23     : RegDef      port map (write_data,'0',clk,L(23),'0',out23 ); --$s7
48      Reg24     : RegDef      port map (write_data,'0',clk,L(24),'0',out24 ); --$t8
49      Reg25     : RegDef      port map (write_data,'0',clk,L(25),'0',out25 ); --$t9
50      Reg26     : RegDef      port map (write_data,'0',clk,L(26),'0',out26 ); --$k0
51      Reg27     : RegDef      port map (write_data,'0',clk,L(27),'0',out27 ); --$k1
52      Reg28     : RegDef      port map (write_data,'0',clk,L(28),'0',out28 ); --$gp
53      Reg29     : RegDef      port map (write_data,'0',clk,L(29),'0',out29 ); --$sp
54      Reg30     : RegDef      port map (write_data,'0',clk,L(30),'0',out30 ); --$fp
55      Reg31     : RegDef      port map (write_data,'0',clk,L(31),'0',out31 ); --$ra
```


At the end, we created two 32x1 multiplexers, each taking the out0 till the out31 signals as the 32 inputs of the multiplexer, but for the first multiplexer, the selector will be read\_sel1 and the output will be data1, and for the second multiplexer, the selector will be read\_sel2 and the output will be data2. This will be used in the reading process of data 1 and data 2.

```

56
57     FirstMux  : Mux32x1 port map (read_sel1, out0, out1, out2, out3, out4, out5, out6,
58
59     SecondMux : Mux32x1 port map (read_sel2, out0, out1, out2, out3, out4, out5, out6,
60
, out7, out8, out9, out10, out11, out12, out13, out14, out15, out16, out17, out18, out19,
, out7, out8, out9, out10, out11, out12, out13, out14, out15, out16, out17, out18, out19,
out20, out21, out22, out23, out24, out25, out26, out27, out28, out29, out30, out31, data1) :
out20, out21, out22, out23, out24, out25, out26, out27, out28, out29, out30, out31, data2) :

```

## The MIPS Register RTL Schematic

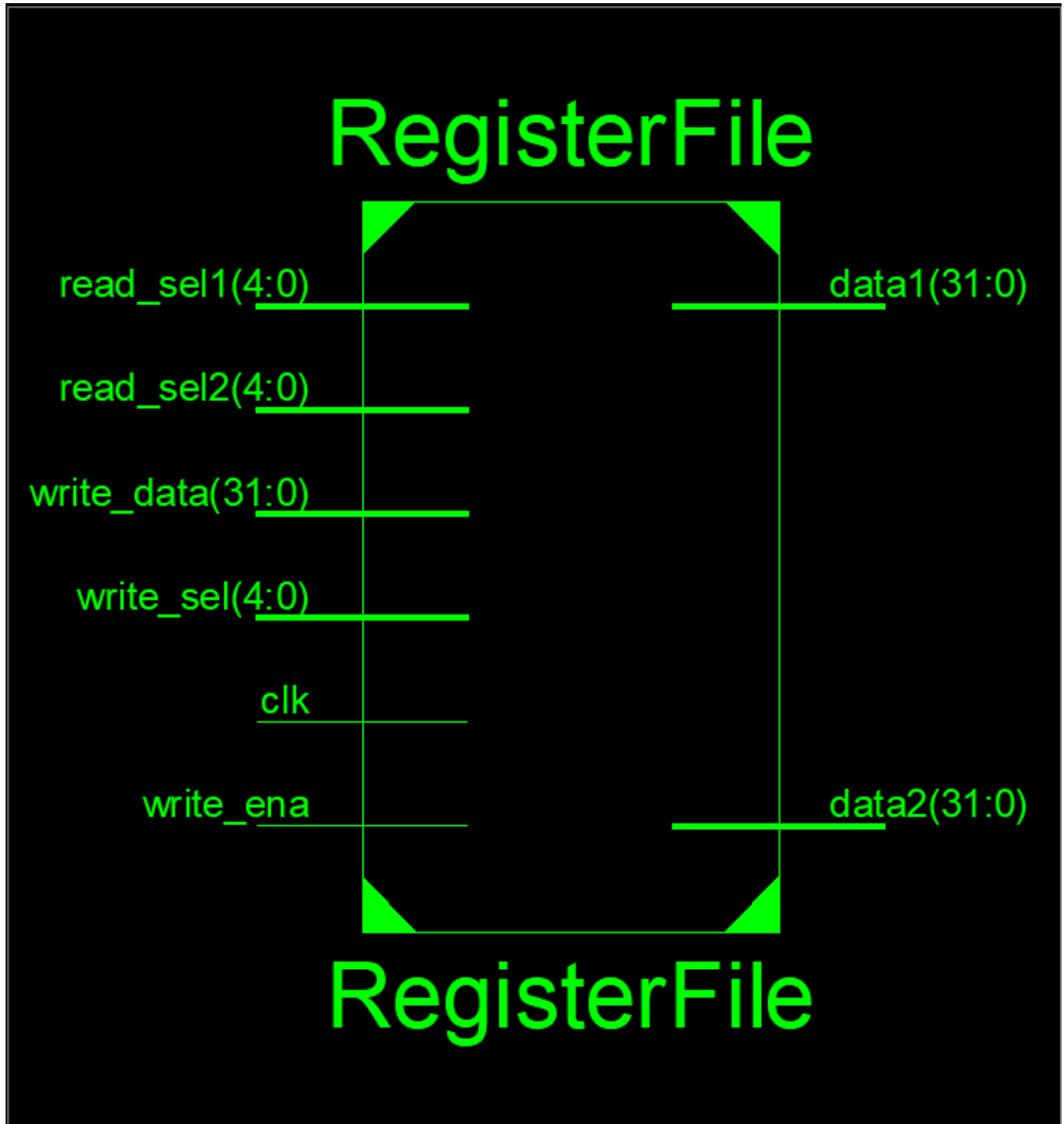

## The MIPS Register Testbench Code


```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY RegisterFileTest IS
5  END RegisterFileTest;
6
7  ARCHITECTURE behavior OF RegisterFileTest IS
8
9      COMPONENT RegisterFile
10     PORT (
11         read_sel1 : IN  std_logic_vector(4 downto 0);
12         read_sel2 : IN  std_logic_vector(4 downto 0);
13         write_sel  : IN  std_logic_vector(4 downto 0);
14         write_ena  : IN  std_logic;
15         clk        : IN  std_logic;
16         write_data : IN  std_logic_vector(31 downto 0);
17         datal      : OUT std_logic_vector(31 downto 0);
18         data2      : OUT std_logic_vector(31 downto 0)
19     );
20     END COMPONENT;
21
22
23     signal read_sel1 : std_logic_vector(4 downto 0) := (others => '0');
24     signal read_sel2 : std_logic_vector(4 downto 0) := (others => '0');
25     signal write_sel  : std_logic_vector(4 downto 0) := (others => '0');
26     signal write_ena  : std_logic := '0';
27     signal clk        : std_logic := '0';
28     signal write_data : std_logic_vector(31 downto 0) := (others => '0');
29
30     signal datal : std_logic_vector(31 downto 0);
31     signal data2 : std_logic_vector(31 downto 0);
32
33     constant clk_period : time := 10 ps;
34
35 BEGIN
36
37     uut: RegisterFile PORT MAP (
38         read_sel1 => read_sel1,
39         read_sel2 => read_sel2,
40         write_sel  => write_sel,
41         write_ena  => write_ena,
42         clk        => clk,
43         write_data => write_data,
44         datal      => datal,
45         data2      => data2
46     );
47
```

```


47
48 clk_process :process
49 begin
50     clk <= '0';
51     wait for clk_period/2;
52     clk <= '1';
53     wait for clk_period/2;
54 end process;
55
56
57 -- Stimulus process
58 stim_proc: process
59 begin
60     wait for clk_period - 3 ps;
61
62     --Write value in $t0
63     write_sel <= "01000" ; --$t0
64     write_data <= "00001111000011110000111100001111" ;
65     write_ena <= '1' ;
66     wait for clk_period * 1;
67
68     --Write value in $s0
69     write_sel <= "10000" ; --$s0
70     write_data <= "11110000111100001111000011110000" ;
71     write_ena <= '1' ;
72     wait for clk_period * 1;
73
74     --Read data from $t0 and $s0
75     read_sel1 <= "01000" ; --$t0
76     read_sel2 <= "10000" ; --$s0
77     write_ena <= '0' ;
78     wait for clk_period * 2;
79
80     report "Test1";
81     assert(data1 = "00001111000011110000111100001111") report "1:Fail" severity error;
82     report "Test2";
83     assert(data2 = "11110000111100001111000011110000") report "2:Fail" severity error;
84
85     wait for clk_period * 1 ;
86
87     --Read data from $t0 and $s0 and write new data in $t0
88     read_sel1 <= "01000" ; --$t0
89     read_sel2 <= "10000" ; --$s0
90     write_sel <= "01000" ; --$t0
91     write_data <= "00000000000000000000000000000000" ;
92     write_ena <= '1' ;
93
94     --
95
96     wait for clk_period * 2;
97
98     report "Test3";
99     assert(data1 = "00000000000000000000000000000000") report "3:Fail" severity error;
100    report "Test4";
101    assert(data2 = "11110000111100001111000011110000") report "4:Fail" severity error;
102    report "Test Complete";
103
104    wait;
105 end process;
106
107 END;

```


## The MIPS Register Sample Output

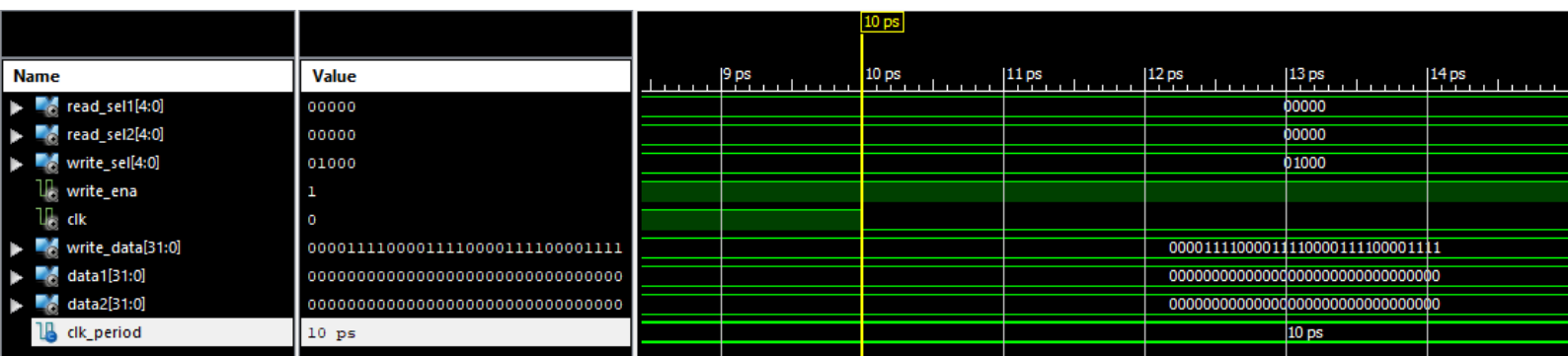

 
At 10 ps, the write\_ena was equal to ‘1’ and the write\_sel was equal to “01000” and the write\_data was equal to “00001111000011110000111100001111”. This means that the 32-bits placed in write\_data should be written to the register of the address equal to “01000”.



 At 20 ps, the write\_ena was equal to ‘1’ and the write\_sel was equal to “10000” and the write\_data was equal to “11110000111100001111000011110000”. This means that the 32-bits placed in write\_data should be written to the register of the address equal to “01000”.



At 30 ps, the write\_ena changed to be equal to ‘0’ which means no writing will occur at this step. Also, at the same time the read\_sel1 changed to be equal to “01000” and read\_sel2 changed to be equal to “10000”. This means that reading process will occur and the previously written two values in the previous page will now be read from the equivalent registers and produced as outputs in data1 and data2 respectively. Consequently, data1 is now equal to “00001111000011110000111100001111” and data2 is equal to “11110000111100001111000011110000”.

 

At 70 ps, the write\_ena changed to be equal to '1' again which means a writing process will take place. However, read\_sel1 was equal to "01000" and read\_sel2 was equal to "10000". Accordingly, writing and reading processes will occur simultaneously. The writing will occur to the register corresponding to the write\_sel equal to "01000" with write\_data equal to "00000000000000000000000000000000". While for the reading process, it will happen to the following two registers with addresses read\_sel1 "01000" and read\_sel2 "10000" respectively. Consequently, data1 is equal to "00000000000000000000000000000000" which was just written and data2 was equal to "11110000111100001111000011110000" which was previously written in previous steps.



## The ALU Register Description

For the second part of phase 1, it was implementing a 32-Bit Full ALU. Firstly, we declared the entity as requested in the project description document.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_signed.all;
4
5  entity ALU is
6
7      Port ( data1      : in  STD_LOGIC_VECTOR (31 downto 0);
8            data2      : in  STD_LOGIC_VECTOR (31 downto 0);
9            aluop       : in  STD_LOGIC_VECTOR (3 downto 0);
10           cin        : in  STD_LOGIC;
11           dataout     : out STD_LOGIC_VECTOR (31 downto 0);
12           cflag       : out STD_LOGIC;
13           zflag       : out STD_LOGIC;
14           oflag       : out STD_LOGIC);
15
16
17  end ALU;
```

Secondly, we began in writing the architecture of the ALU. We decided to implement the ALU using processes and variables, and we will use the case and for loop. At the beginning, we wrote the process sensitivity list of (data1,data2,aluop,cin) to make the results reassessed whenever one of these four inputs experiences a change. We declared the following variables : temp (with size of n downto 0 – 32 downto 0) which will be used in the addition and subtraction processes, outvariable (with size of n-1 downto 0 – 31 downto 0) which will be used to store the final results of the functions of the ALU, cintemp which will be used to store the carry in of the addition and subtraction processes, cvariable for the carry out of the addition and subtraction processes, and finally zvariable which will be used to check if the result of the requested function is equal to zero or not. Also, we initialized the cflag, oflag, temp, zvariable all with zeros.

```

18
19 architecture Behavioral of ALU is
20
21 begin
22
23     process(data1,data2,aluop,cin)
24     variable temp : STD_LOGIC_VECTOR (32 downto 0);
25     variable outvariable : STD_LOGIC_VECTOR (31 downto 0);
26
27     variable cvariable, zvariable, cintemp : STD_LOGIC;
28     BEGIN
29         cflag <= '0';
30         oflag <= '0';
31         temp := "00000000000000000000000000000000";
32         zvariable := '0';

```

Then, we started in writing the case process with “case aluop” for different actions to be taken based on the value of the aluop. The first case is the addition when the aluop = “0010”. Then, the cintemp will be equal to the value of the cin. The temp will be equal to the result of the sum of data1 and data2 and cintemp (carry input if there is carry input by the user), however, data1 and data2 are not summed directly, both data1 and data2 are concatenated with ‘0’ at the most significant bit to increase the size from 32 bit to 33 bits temporarily to provide an extra bit empty for holding any carry out. Moreover, the outvariable will be equal to the temp taking only the first 32 bits and the 33th bit will be placed in the cvariable. For the oflag (overflow flag), we wrote the equation found in the screenshot to detect the overflow which happens if two large numbers are added greater than the value that the software could process resulting in an unexpected answer with an unexpected sign, overflow happens for example when adding two large positive numbers and the result turns out to be negative or adding two negative numbers and the results turns out to be positive. Finally, the cflag is assigned to hold the value of the cvariable. The subtraction is the same case of the addition as we implemented the subtraction to be carried out using addition of the 2’s complement instead of direct subtraction, and it happens when the aluop is equal to “0110” along with the cintemp equal to ‘1’ and with a subtraction operand instead.




Next, we constructed a for loop that basically checks for all the bits of the outvariable starting for the bit no. 0 to the bit no. 31 if they are all equal to zero by making an “OR” operation with the zvariable which was initialized previously by zero. If all the bits are zeros, the zvariable will remain equal to 0.

```
--zero output check--  
for i in 0 to 31 loop  
    zvariable := zvariable or outvariable(i);  
end loop;  
-----
```

At the end, dataout is assigned to hold the contents of the outvariable and the zflag is assigned to hold the opposite of the zvariable to be equal to ‘1’ when all the bits are equal to ‘0’ and vice versa.

```
dataout <= outvariable;  
zflag <= not zvariable;  
  
END PROCESS;
```

## The ALU RTL Schematic

 

## The ALU Testbench Code

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4
5  ENTITY ALUTest IS
6  END ALUTest;
7
8  ARCHITECTURE behavior OF ALUTest IS
9
10
11     COMPONENT ALU
12     PORT (
13         data1 : IN  std_logic_vector(31 downto 0);
14         data2 : IN  std_logic_vector(31 downto 0);
15         aluop : IN  std_logic_vector(3 downto 0);
16         cin : IN  std_logic;
17         dataout : OUT std_logic_vector(31 downto 0);
18         cflag : OUT std_logic;
19         zflag : OUT std_logic;
20         oflag : OUT std_logic
21     );
22     END COMPONENT;
23
24
25     signal data1 : std_logic_vector(31 downto 0) := (others => '0');
26     signal data2 : std_logic_vector(31 downto 0) := (others => '0');
27     signal aluop : std_logic_vector(3 downto 0) := (others => '0');
28     signal cin : std_logic := '0';
29
30     signal dataout : std_logic_vector(31 downto 0);
31     signal cflag : std_logic;
32     signal zflag : std_logic;
33     signal oflag : std_logic;
34
35
36 BEGIN
37
38     uut: ALU PORT MAP (
39         data1 => data1,
40         data2 => data2,
41         aluop => aluop,
42         cin => cin,
43         dataout => dataout,
44         cflag => cflag,
45         zflag => zflag,
46         oflag => oflag
47     );
```

```

48
49
50
51 -- Stimulus process
52     stim_proc: process
53 begin
54     cin <= '0';
55     wait for 10 ns;
56     --AND testcasel
57     data1 <= "11000000000000000000000000000000" ;
58     data2 <= "10100000000000000000000000000000" ;
59     aluop <= "0000" ;
60     wait for 10 ns;
61     report "Test1";
62     assert(dataout = "10000000000000000000000000000000" and zflag = '0') report "1:Fail" severity error;
63
64     wait for 1 ns;
65
66     --AND testcase2
67     data1 <= x"0F0F0F0F";
68     data2 <= x"F0F0F0FF";
69     aluop <= "0000" ;
70     wait for 10ns;
71     report "Test2";
72     assert(dataout = x"0000000F" and zflag = '0') report "2:Fail" severity error;
73
74     wait for 1 ns;
75
76     --OR testcasel
77     data1 <= "11000000000000000000000000000000" ;
78     data2 <= "10100000000000000000000000000000" ;
79     aluop <= "0001" ;
80     wait for 10 ns;
81     report "Test3";
82     assert(dataout = "11100000000000000000000000000000" and zflag = '0') report "3:Fail" severity error;
83
84     wait for 1 ns;
85

```

```

85
86 --OR testcase2
87     data1 <= x"0F0F0F0F";
88     data2 <= x"F0F0F0FF";
89     aluop <= "0001" ;
90     wait for 10ns;
91     report "Test4";
92     assert(dataout = x"FFFFFFF" and zflag = '0') report "5:Fail" severity error;
93
94     wait for 1 ns;
95
96 --NOR testcasel
97     data1 <= "11000000000000000000000000000000" ;
98     data2 <= "10100000000000000000000000000000" ;
99     aluop <= "1100" ;
100    wait for 10 ns;
101    report "Test6";
102    assert(dataout = "00011111111111111111111111111111" and zflag = '0') report "6:Fail" severity error;
103
104    wait for 1 ns;
105
106 --NOR testcase2
107    data1 <= x"0F0F0F0F";
108    data2 <= x"F0F0F0FF";
109    aluop <= "1100" ;
110    wait for 10ns;
111    report "Test7";
112    assert(dataout = x"00000000" and zflag = '1') report "7:Fail" severity error;
113
114    wait for 1 ns;
115
116 --ADD testcasel (overflow = 1, cout = 0)
117    data1 <= "01110000000000000000000000000000" ;
118    data2 <= "01100000000000000000000000000000" ;
119    aluop <= "0010" ;
120    wait for 10 ns;
121    report "Test8";
122    assert(dataout = "11010000000000000000000000000000" and oflag = '1' and cflag = '0' and zflag = '0') report "8:Fail" severity error;
123
124    wait for 1 ns;
125

```

```

125
126 --ADD testcase2 (zero = 1, cout = 1)
127     data1 <= "11110000000000000000000000000000" ;
128     data2 <= "00010000000000000000000000000000" ;
129     aluop <= "0010" ;
130     wait for 10 ns;
131     report "Test9";
132     assert(dataout = "00000000000000000000000000000000" and oflag = '0' and cflag = '1' and zflag = '1') report "9:Fail" severity error;
133
134     wait for 1 ns;
135
136 --ADD testcase3 (cout = 0)
137     data1 <= x"00000009";
138     data2 <= x"0000000A";
139     aluop <= "0010" ;
140     wait for 10ns;
141     report "Test10";
142     assert(dataout = "00000000000000000000000000000000" and oflag = '0' and cflag = '0' and zflag = '0') report "10:Fail" severity error;
143
144     wait for 1 ns;
145
146 --ADD testcase4 (cout = 1)
147     data1 <= x"FFFFFFF9";
148     data2 <= x"FFFFFFFA";
149     aluop <= "0010" ;
150     wait for 10ns;
151     report "Test11";
152     assert(dataout = "11111111111111111111111111110011" and oflag = '0' and cflag = '1' and zflag = '0') report "11:Fail" severity error;
153
154     wait for 1 ns;
155
156 --ADD testcase5 (overflow =1 cout = 0)
157     data1 <= x"7FFFFFFF";
158     data2 <= x"7FFFFFFF";
159     aluop <= "0010" ;
160     wait for 10ns;
161     report "Test12";
162     assert(dataout = "1111111111111111111111111111110" and oflag = '1' and cflag = '0' and zflag = '0') report "12:Fail" severity error;
163
164     wait for 1 ns;

```

```

165
166 --SUB testcase1 (cout = 0)
167     data1 <= "00000000000000000000000000000011" ; --a = 7
168     data2 <= "000000000000000000000000000000110" ; --b = 6
169     cin <= '1';
170     aluop <= "0110" ;
171     wait for 10 ns;
172     report "Test13";
173     assert(dataout = "00000000000000000000000000000001" and oflag = '0' and cflag = '0' and zflag = '0') report "13:Fail" severity error;
174
175     wait for 1 ns;
176
177 --SUB testcase2 (cout = 1)
178     data1 <= "000000000000000000000000000000110" ; --a = 6
179     data2 <= "000000000000000000000000000000111" ; --b = 7
180     aluop <= "0110" ;
181     wait for 10 ns;
182     report "Test14";
183     assert(dataout = "1111111111111111111111111111111" and oflag = '0' and cflag = '1' and zflag = '0') report "14:Fail" severity error;
184
185     wait for 1 ns;
186
187 --SUB testcase3 (zero = 1, cout = 0)
188     data1 <= "000000000000000000000000000000110" ; --a = 6
189     data2 <= "000000000000000000000000000000110" ; --b = 6
190     aluop <= "0110" ;
191     wait for 10ns;
192     report "Test15";
193     assert(dataout = "00000000000000000000000000000000" and oflag = '0' and cflag = '0' and zflag = '1') report "15:Fail" severity error;
194
195     wait for 1 ns;
196
197 --SUB testcase4 (cout = 1)
198     data1 <= "000000000000000000000000000000110" ; --a = 6
199     data2 <= "11111111111111111111111111111010" ; --b = -6
200     aluop <= "0110" ;
201     wait for 10ns;
202     report "Test16";
203     assert(dataout = "0000000000000000000000000000001100" and oflag = '0' and cflag = '1' and zflag = '0') report "16:Fail" severity error;
204
205     wait for 1 ns;

```




```


205     wait for 1 ns;
206
207 --SUB testcase5 (cout = 0)
208     data1 <= x"00000000C";
209     data2 <= x"00000000A";
210     aluop <= "0110" ;
211     wait for 10ns;
212     report "Test17";
213     assert(dataout = "0000000000000000000000000000010" and oflag = '0' and cflag = '0' and zflag = '0') report "17:Fail" severity error;
214
215     wait for 1 ns;
216
217 --SUB testcase6 (cout = 1)
218     data1 <= x"FFFFFFF9";
219     data2 <= x"FFFFFFFA";
220     aluop <= "0110" ;
221     wait for 10ns;
222     report "Test18";
223     assert(dataout = "1111111111111111111111111111111" and oflag = '0' and cflag = '1' and zflag = '0') report "18:Fail" severity error;
224
225     wait for 1 ns;
226
227 --SUB testcase7 (zero = 1, cout = 0)
228     data1 <= x"00000001";
229     data2 <= x"00000001";
230     aluop <= "0110" ;
231     wait for 10ns;
232     report "Test19";
233     assert(dataout = "0000000000000000000000000000000" and oflag = '0' and cflag = '0' and zflag = '1') report "19:Fail" severity error;
234
235     wait for 1 ns;
236
237     report "Test Complete";
238
239     wait;
240 end process;
241
242 END;
243

```


## The ALU Sample Output

 

 
At 30,410 ps, the aluop was equal to “0000”, accordingly, “AND” operation should be performed. Data1 was equal to “0f0f0f0f” and data 2 was equal to “f0f0f0f0” both in hexadecimal. Dataout was equal to “0000000f” which was expected and is correct.



 
At 44,442 ps, the aluop was equal to “0001”, accordingly, “OR” operation should be performed. Data1 was equal to “0f0f0f0f” and data 2 was equal to “f0f0f0f0” both in hexadecimal. Dataout was equal to “ffffff” which is expected and correct.



 
At 66,042 ps, the aluop was equal to “1100”, accordingly, “NOR” operation should be performed. Data1 was equal to “0f0f0f0f” and data 2 was equal to “f0f0f0f0” both in hexadecimal. Dataout was equal to “00000000” which is expected and correct.



 
At around 85,200 ps, the aluop was equal to “0010”, accordingly, “Addition” operation should be performed. Data1 was equal to a very large positive number and data2 was equal to a very large positive number. The dataout was equal to a very large negative number which is an error and the case of overflowing, accordingly the oflag was equal to 1.



 
At 107,810 ps, the aluop was equal to “0010”, accordingly, “Addition” operation should be performed. Data1 was equal to “9” and data2 was equal to “10” both in signed decimals. Dataout was equal to “19” and all the three flags were equal to zero which is expected and correct.



 
At 117,380 ps, the aluop was equal to “0010”, accordingly, “Addition” operation should be performed. Data1 was equal to “-7” and data2 was equal to “-6” both in signed decimals. Dataout was equal to “-13” with the cflag is equal to ‘1’ indicating that there has been a carry out while the rest two flags were equal to zero which is expected and correct.



 At 138,516 ps, the aluop was equal to “0110”, accordingly, “Subtraction” operation should be performed. Data1 was equal to “7” and data2 was equal to “6” both in signed decimals. Dataout was equal to “1” with all the three flags equal to zero which is expected and correct.



 At 150 ps, the aluop was equal to “0110”, accordingly, “Subtraction” operation should be performed. Data1 was equal to “6” and data2 was equal to “7” both in signed decimals. Dataout was equal to “-1” with the cflag is equal to ‘1’ indicating that there has been a carry out while the rest two flags were equal to zero which is expected and correct.




At 155,256 ps, the aluop was equal to “0110”, accordingly, “Subtraction” operation should be performed. Data1 was equal to “6” and data2 was equal to “6” both in signed decimals. Dataout was equal to “0” with the zflag is equal to ‘1’ indicating that the output is equal to zero while the rest two flags were equal to zero which is expected and correct.

# Phase 2
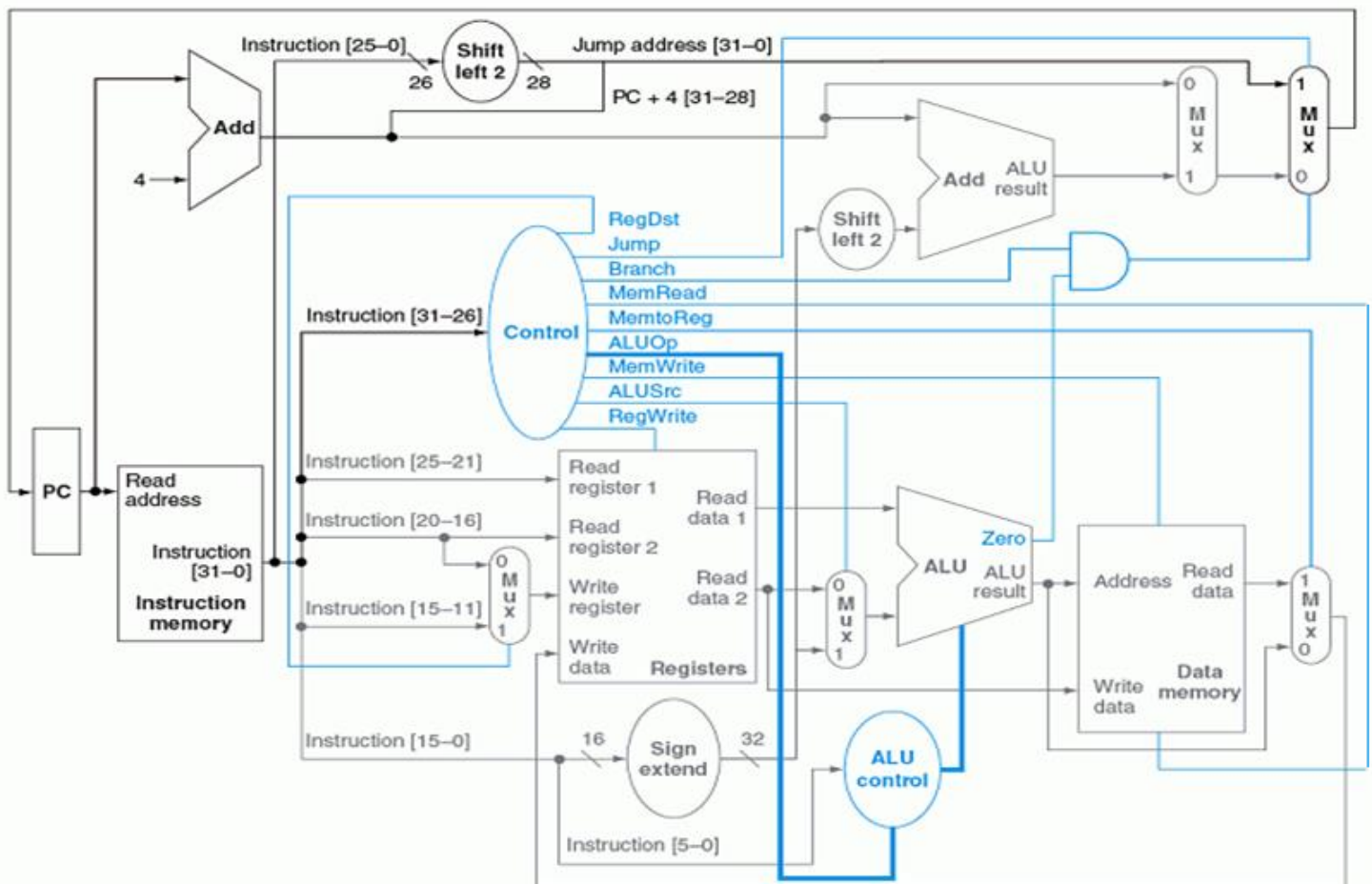
## The MIPS CPU Description

In phase 2, it was required to design a simple MIPS CPU. The proposed CPU should be able to perform certain instructions: R-type (AND, OR, ADD, SUB, SLT and NOR), I-type (lw, sw, beq, bne) and J instruction. To make this cpu, we will need to design every single module found in this diagram as an alone module and then use all these modules to make the main module required of the MIPS CPU.





Firstly, we designed the “PC” module which takes three inputs and produces one output. The three inputs are the following: “CLK”, “RESET”, “Address” and the only output is “PC”. The “Address” and the “PC” are both buses with 32 bits, while the “CLK” and the “RESET” are only one bit. Followingly, we created a signal named “instructionAddress” to be used as a buffer inside the process instead of directly using the output and then the signal will be assigned to the output at the end. The architecture of the PC is simple as it is a process which we named “PC\_Process” with “CLK” and “RESET” in the sensitivity list. It functions by placing the input “Address” into the signal “instructionAddress” (substitute of the output) at the rising edge of the clock, but if the “RESET” happens to be equal to ‘1’, then the “instructionAddress” will be reset and the whole 32 bits will be zeros.



```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity PC is
5      port(
6          signal CLK, RESET : in std_logic;
7          signal Address      : in std_logic_vector(31 downto 0);
8          signal PC           : out std_logic_vector(31 downto 0)
9      );
10 end PC;
11
12
13 architecture Behavioral of PC is
14     signal instructionAddress : std_logic_vector(31 downto 0) := X"00000000";
15
16     begin
17
18         PC_Process : process(CLK, RESET)
19             begin
20
21                 if RISING_EDGE(CLK) then
22                     instructionAddress <= Address;
23                 end if;
24
25                 if RESET = '1' then
26                     instructionAddress <= X"00000000";
27                 end if;
28             end process;
29
30             PC <= instructionAddress;
31 end Behavioral ;


```

Secondly, we designed the “Adder4” module that increments the output coming from the PC module by 4, it takes one input and produces one output where both are of size 32 bits. The architecture is simple where “Output” will be equal to “Input + 4” and we included the “Numeric\_STD” library in order to use the “signed” function needed for the addition.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity Adder4 is
6      Port ( Input  : in  STD_LOGIC_VECTOR (31 downto 0);
7            Output  : out STD_LOGIC_VECTOR (31 downto 0));
8  end Adder4;
9
10 architecture Behavioral of Adder4 is
11
12 begin
13
14     Output <= STD_LOGIC_VECTOR(signed(Input) + 4);
15
16 end Behavioral;
17
18

```

 

Thirdly, we designed the “ShiftLeft2” module that shifts the input received by 2 bits from the left side but with preserving the sign-bit. It takes one input and produces one output where both are of size 32 bits. The architecture is simple where the 32th bit of the “Output” ( Output (31) ) will be equal to the 32th bit of the “Input” ( Input (31) ) which is the step of preserving the sign-bit. Then, three bits are skipped from the input to do the shifting operation by skipping the already transferred sign-bit (the 32th bit) and the 2 bits of the shifting which will be the 31<sup>st</sup> and the 30<sup>th</sup> bits, followingly, starting from the 29<sup>th</sup> bit till the 0<sup>th</sup> bit of the input ( Input (28 downto 0) ) will be transferred to the output to represent the 31<sup>st</sup> bit to the 3<sup>rd</sup> bit ( Output (30 downto 2) ). Accordingly, the output is produced but with the 1<sup>st</sup> and 0<sup>th</sup> bit unassigned ( Output (1 downto 0) ) which will be filled with zeros according to the rules of shifting.





```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity ShiftLeft2 is
5      Port ( Input  : in  STD_LOGIC_VECTOR (31 downto 0);
6            Output  : out STD_LOGIC_VECTOR (31 downto 0));
7  end ShiftLeft2;
8
9  architecture Behavioral of ShiftLeft2 is
10 begin
11
12     Output(31)          <= Input(31);
13     Output(30 downto 2) <= Input(28 downto 0);
14     Output(1 downto 0)  <= (Others => '0');
15
16 end Behavioral;

```

Fourthly, we designed two multiplexers, both multiplexers are 2x1 Mux receiving two inputs, one-bit selection line and producing one output. The two multiplexers are the same architecture and function, but one was designed to receive 32-bits inputs producing one 32-bits output and the other receives 5-bits inputs producing one 5-bits output instead. This is because all multiplexers used in the CPU are working with 32-bits basis but the multiplexer whose output goes into the “WriteRegister” which receives the address of the register for the data to be written into is 5-bits. The two multiplexers are named “CPUMux” and “5x1Mux” (5x1 was used just to indicate that it receives 5-bits and produces 1 output) respectively. The architecture is easy where the output will be determined based on the selection line which is named “Selector” in “CPUMux” and named ‘S’ in “5x1Mux”, if the selection line is equal to ‘0’, the output will be equal to the input “i0”, and if the selection line is equal to ‘1’, the output will be equal to the input “i1” while all other cases will produce 32 Z’s.

  

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity CPUMux is
5      Port ( Selector : in  STD_LOGIC;
6            i0        : in  STD_LOGIC_VECTOR (31 downto 0);
7            i1        : in  STD_LOGIC_VECTOR (31 downto 0);
8            Output     : out STD_LOGIC_VECTOR (31 downto 0));
9  end CPUMux;
10
11 architecture Behavioral of CPUMux is
12
13 begin
14
15     Output <= i0 when Selector = '0' else
16             i1 when Selector = '1' else
17             (others => 'Z');
18
19 end Behavioral;


```

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Mux5x1 is
5      Port ( S        : in  STD_LOGIC;
6            i0        : in  STD_LOGIC_VECTOR (4 downto 0);
7            i1        : in  STD_LOGIC_VECTOR (4 downto 0);
8            output     : out STD_LOGIC_VECTOR (4 downto 0));
9  end Mux5x1;
10
11 architecture Behavioral of Mux5x1 is
12
13 begin
14
15     output <= i0  when S = '0' else
16             i1  when S = '1' else
17             (others => 'Z');
18
19 end Behavioral;

```

Fifthly, we designed the “SignExtend” module that does what it actually says by receiving a 16-bit input and extend its sign to produce a 32-bit output where the 16 bits difference is a repetition of the sign-bit. How it works is as the two lines written in the architecture where it checks the sign-bit of the input which the 16<sup>th</sup> bit ( Input (15) ), if the sign-bit is ‘1’, then the output will be equal to input but concatenated with 16 ones to the left side of the input, however, if the sign-bit is ‘0’, the output will be equal to the input concatenated with 16 zeros the left side of the input and any other case will produce Zs.

 


```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity SignExtend is
5      Port ( Input  : in  STD_LOGIC_VECTOR (15 downto 0);
6            Output  : out STD_LOGIC_VECTOR (31 downto 0));
7  end SignExtend;
8
9  architecture Behavioral of SignExtend is
10 begin
11
12     Output <= "0000000000000000" & Input WHEN Input(15) = '0' ELSE
13         "1111111111111111" & Input WHEN Input(15) = '1' ELSE
14         (Others => 'Z');
15
16
17 end Behavioral;

```

 Moving on to the 6<sup>th</sup> module, we made a module named “JumpAddressConcat” which will be responsible for creating the jump address by the concatenation of the last 4 bits from the output of the “Adder4” module (PC + 4) ( InputLeft (31 downto 28) ) to the first 28 bits of the output from shifting left 2 of the instruction ( InputRight (27 downto 0) ).




```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity JumpAddressConcat is
5      Port ( InputLeft  : in  STD_LOGIC_VECTOR (31 downto 0);
6            InputRight : in  STD_LOGIC_VECTOR (31 downto 0);
7            Output     : out STD_LOGIC_VECTOR (31 downto 0));
8  end JumpAddressConcat;
9
10 architecture Behavioral of JumpAddressConcat is
11 begin
12
13     Output <= InputLeft(31 downto 28) & InputRight(27 downto 0);
14
15 end Behavioral;

```

For the 7<sup>th</sup> module, it will be the “MainControlUnit” which is responsible for controlling the CPU, it takes only one 6-bit input and produces 9 outputs where all outputs are a single bit except the “ALUOp” output will be 2 bits. The input is the OpCode which the last 6 bits of the instruction loaded (instruction [31-26] ). The eight single bit outputs are the following: MemRead, MemWrite, RegDst, Branch, MemtoReg, ALUSrc, Jump and RegWrite. The “MainControlUnit” was using the case process format where cases are based on the following truth table which could be found in Lecture 10.

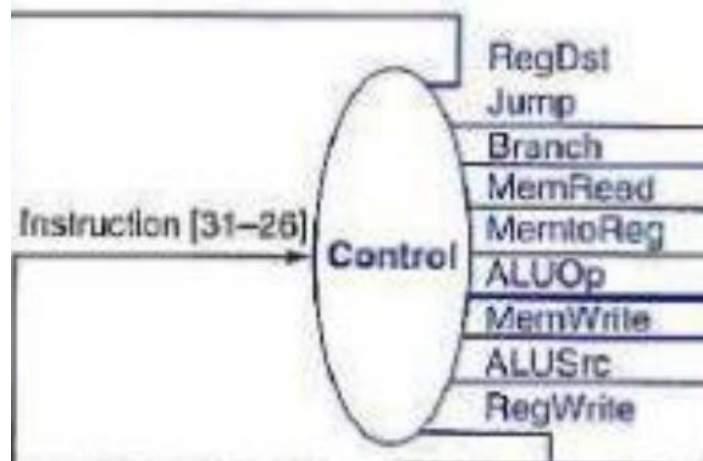

| Control | Signal name | R-format | lw | sw | beq |
|---------|-------------|----------|----|----|-----|
| Inputs  | Op5         | 0        | 1  | 1  | 0   |
|         | Op4         | 0        | 0  | 0  | 0   |
|         | Op3         | 0        | 0  | 1  | 0   |
|         | Op2         | 0        | 0  | 0  | 1   |
|         | Op1         | 0        | 1  | 1  | 0   |
|         | Op0         | 0        | 1  | 1  | 0   |
| Outputs | RegDst      | 1        | 0  | X  | X   |
|         | ALUSrc      | 0        | 1  | 1  | 0   |
|         | MemtoReg    | 0        | 1  | X  | X   |
|         | RegWrite    | 1        | 1  | 0  | 0   |
|         | MemRead     | 0        | 1  | 0  | 0   |
|         | MemWrite    | 0        | 0  | 1  | 0   |
|         | Branch      | 0        | 0  | 0  | 1   |
|         | ALUOp1      | 1        | 0  | 0  | 0   |
|         | ALUOp0      | 0        | 0  | 0  | 1   |

However, the jump process and the bne were not in this table. In the case of the bne, the outputs are exactly like the beq process, but the opcode is different as the bne opcode is “000101”. For the jump, the opcode will be equal to “000010” all the outputs are zeros except for the RegDst and the MemtoReg will be don’t cares (‘X’) and obviously the jump output will be equal to ‘1’. For any other cases, all the outputs will be reset and equal to zeros.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity MainControlUnit is
5
6      Port ( OpCode      : in  STD_LOGIC_VECTOR (5 downto 0);
7            MemRead      : out STD_LOGIC;
8            MemWrite     : out STD_LOGIC;
9            RegDst       : out STD_LOGIC;
10           Branch       : out STD_LOGIC;
11           MemtoReg      : out STD_LOGIC;
12           ALUSrc        : out STD_LOGIC;
13           ALUOp         : out STD_LOGIC_VECTOR (1 downto 0);
14           Jump          : out STD_LOGIC;
15           RegWrite      : out STD_LOGIC);
16
17 end MainControlUnit;
18
19 architecture Behavioral of MainControlUnit is
20 begin
21
22     Process (OpCode)
23     BEGIN
24
25         RegWrite <= '0';
26
27         CASE OpCode IS
28
29             -----RType-----
30             WHEN "000000" =>
31                 MemRead  <= '0' ;
32                 MemWrite <= '0' ;
33                 RegDst   <= '1' ;
34                 Branch   <= '0' ;
35                 MemtoReg <= '0' ;
36                 ALUSrc   <= '0' ;
37                 ALUOp    <= "10" ;
38                 Jump     <= '0' ;
39                 RegWrite <= '1' ;
40             -----
41

```



```

41
42 -----LW-----
43 WHEN "100011" =>
44     MemRead    <= '1' ;
45     MemWrite   <= '0' ;
46     RegDst     <= '0' ;
47     Branch     <= '0' ;
48     MemtoReg   <= '1' ;
49     ALUSrc     <= '1' ;
50     ALUOp      <= "00" ;
51     Jump       <= '0' ;
52     RegWrite   <= '1' ;
53 -----
54
55 -----SW-----
56 WHEN "101011" =>
57     MemRead    <= '0' ;
58     MemWrite   <= '1' ;
59     RegDst     <= 'X' ;
60     Branch     <= '0' ;
61     MemtoReg   <= 'X' ;
62     ALUSrc     <= '1' ;
63     ALUOp      <= "00" ;
64     Jump       <= '0' ;
65     RegWrite   <= '0' ;
66 -----
67
68 -----beq-----
69 WHEN "000100" =>
70     MemRead    <= '0' ;
71     MemWrite   <= '0' ;
72     RegDst     <= 'X' ;
73     Branch     <= '1' ;
74     MemtoReg   <= 'X' ;
75     ALUSrc     <= '0' ;
76     ALUOp      <= "01" ;
77     Jump       <= '0' ;
78     RegWrite   <= '0' ;
79 -----


```

```

80
81      -----bne-----
82      WHEN "000101" =>
83          MemRead    <= '0' ;
84          MemWrite   <= '0' ;
85          RegDst     <= 'X' ;
86          Branch     <= '1' ;
87          MemtoReg   <= 'X' ;
88          ALUSrc     <= '0' ;
89          ALUOp      <= "01" ;
90          Jump       <= '0' ;
91          RegWrite   <= '0' ;
92      -----
93
94
95      -----Jump-----
96      WHEN "000010" =>
97          MemRead    <= '0' ;
98          MemWrite   <= '0' ;
99          RegDst     <= 'X' ;
100         Branch     <= '0' ;
101         MemtoReg   <= 'X' ;
102         ALUSrc     <= '0' ;
103         ALUOp      <= "00" ;
104         Jump       <= '1' ;
105         RegWrite   <= '0' ;
106     -----
107
108     WHEN OTHERS => NULL;
109         MemRead    <= '0' ;
110         MemWrite   <= '0' ;
111         RegDst     <= '0' ;
112         Branch     <= '0' ;
113         MemtoReg   <= '0' ;
114         ALUSrc     <= '0' ;
115         ALUOp      <= "00" ;
116         Jump       <= '0' ;
117         RegWrite   <= '0' ;
118
119
120     END CASE;
121
122     END PROCESS;
123
124
125 end Behavioral;

```

Next was the “ALUControlUnit”. This module takes in two inputs, the FunctionCode which is 6 bits (it is the function field in the instruction which is the first 6 bits – instruction [5-0] ) and the ALUOp which is 2 bits which is the same ALUOp coming out as an output from the “MainControlUnit”. The output produced is the “ALUFuncnt” of a size of 4 bits which is the ALU Control Lines which will be the input of the ALU to decide which operation to make. The “ALUControlUnit” was designed based on the upcoming truth table.

 

| Instruction<br>OpCode | ALUOp | Instruction<br>Operation | Funct<br>Field | Desired<br>ALU Action | ALU Control<br>Input |
|-----------------------|-------|--------------------------|----------------|-----------------------|----------------------|
| LW                    | 00    | Load Word                | xxxxxx         | Add                   | 0010                 |
| SW                    | 00    | Store Word               | xxxxxx         | Add                   | 0010                 |
| BEQ                   | 01    | Branch Equal             | xxxxxx         | Subtract              | 0110                 |
| BNE                   | 01    | Branch Not<br>Equal      | xxxxxx         | Subtract              | 0110                 |
| R-Type                | 10    | Add                      | 100000         | Add                   | 0010                 |
| R-Type                | 10    | Subtract                 | 100010         | Subtract              | 0110                 |
| R-Type                | 10    | And                      | 100100         | And                   | 0000                 |
| R-Type                | 10    | Or                       | 100101         | Or                    | 0001                 |
| R-Type                | 10    | Set On Less<br>Than      | 101010         | Set On Less<br>Than   | 0111                 |
| R-Type                | 10    | Nor                      | 100111         | Nor                   | 1100                 |

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ALUControlUnit is
    Port ( FunctionCode : in  STD_LOGIC_VECTOR (5 downto 0);
          ALUOp         : in  STD_LOGIC_VECTOR (1 downto 0);
          ALUFuncnt      : out STD_LOGIC_VECTOR (3 downto 0));
end ALUControlUnit;

architecture Behavioral of ALUControlUnit is
begin

ALUFuncnt(3) <= (ALUOp(1) AND FunctionCode(0) AND FunctionCode(1) AND FunctionCode(5));

ALUFuncnt(2) <= ALUOp(0) OR (ALUOp(1) AND FunctionCode(1));

ALUFuncnt(1) <= NOT ALUOp(1) OR ((NOT FunctionCode(2)) AND NOT(FunctionCode(0)));

ALUFuncnt(0) <= (FunctionCode(3) OR FunctionCode(0)) AND (NOT (FunctionCode(1) AND FunctionCode(0))) AND ALUOp(1);

end Behavioral;





```

That leaves us with four components or modules for the CPU which are the Registers, ALU, Data Memory, Instruction Memory. For the Registers and the ALU, we used the previously built modules of “RegisterFile” and “ALU” of Phase 1 but with a small modification to the ALU which is adding the SLT function (Set On Less Than), accordingly, you could refer back to the description of both modules in the “Phase 1” section.

```

70
71 -----slt-----
72 when "0111" =>
73 if (data1<data2) THEN
74 outvariable := x"00000001";
75 else
76 outvariable := x"00000000";
77 end if;
78 -----

```

    

Regarding the data and instruction memories, they were already provided by the doctor, so we used them with only minor edits. For both modules, we removed the generic part and replaced the sizes with direct numbers instead as the whole modules were non-generic, so we decided to complete it that way. However, in the instruction memory, there were some errors regarding the instructions supplied, so we made some more edits. Firstly, we deactivated (by making it in the format of a comment) the last instruction which was originally placed in MEMORY(32) which was a jumping instruction and instead we made MEMORY(32) to hold the binary value of this instruction “add \$s0, \$s0, \$t8” which will be responsible for writing the last value of the sequence which is ‘-1’ in the register \$s0. Also, we added an extra instruction to be MEMORY(33) which is the same instruction in the previous line of MEMORY(32) but this time the goal was not performing the exact instruction itself but was to add any extra instruction with no concern about the instruction contents itself but only an instruction that involves using register \$s0 in order for us to read the new value of \$s0 which was written by the previous instruction.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.all;
3  use IEEE.STD_LOGIC_SIGNED.all;
4  use IEEE.STD_LOGIC_ARITH.all;
5
6  use IEEE.std_logic_textio.all;
7  library STD;
8  use STD.textio.all;
9
10  ----Only removed the generic variables and replaced them with equivalent numbers as the whole cod
11
12  entity INSTRMEMORY is
13
14      port(
15          LoadIt : in Std_logic ;
16          DATA  : out STD_LOGIC_VECTOR(31 downto 0);
17          ADDRESS : in STD_LOGIC_VECTOR(31 downto 0);
18          CLK    : in STD_LOGIC
19      );
20  end INSTRMEMORY;
21
22
23  architecture BEHAVIORAL of INSTRMEMORY is
24      signal ADDRover4: STD_LOGIC_VECTOR(29 downto 0);
25  begin
26
27  ROM_PROCESS: process(CLK, ADDRESS) is
28      type MEM is array(0 to 63) of STD_LOGIC_VECTOR(31 downto 0);
29      variable MEMORY: MEM := (others => X"00000000");
30      variable IADR: INTEGER;
31
32  begin
33

```



```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3 use IEEE.STD_LOGIC_UNSIGNED.all;
4
5 entity DATAMEMORY is
6 ----Only removed the generic variables and replaced them with equivalent values
7     port ( LoadIt      : in STD_LOGIC;
8           INPUT         : in STD_LOGIC_VECTOR (31 downto 0);
9           OUTPUT        : out STD_LOGIC_VECTOR (31 downto 0);
10          MEM_READ       : in STD_LOGIC;
11          MEM_WRITE      : in STD_LOGIC;
12          ADDRESS        : in STD_LOGIC_VECTOR (31 downto 0);
13          CLK            : in STD_LOGIC
14          );
15
16 end DATAMEMORY;
17
18 architecture BEHAVIORAL of DATAMEMORY is
19
20     type    MEM is array (0 to 63) of STD_LOGIC_VECTOR (31 downto 0);
21     signal MEMORY : MEM;
22     signal OUTS: STD_LOGIC_VECTOR(31 downto 0);
23     signal ADDRover4: STD_LOGIC_VECTOR(29 downto 0);
24     signal ADDR_int: integer;
25 begin
26
27     process ( MEM_READ, MEM_WRITE, CLK, ADDRESS, INPUT ) is
28     begin
29         if LoadIt = '1' then
30             -----
31             --Project1 test
32             -----
33             memory(0)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
34             memory(1)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
35             memory(2)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
36             memory(3)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
37             memory(4)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
38             memory(5)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
39             memory(6)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
40             memory(7)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
41             memory(8)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
42             memory(9)   <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
43             memory(10)  <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
44             memory(11)  <= "XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX" ;
45             memory(12)  <= "00000000000000000000000000000001100" ;
46             memory(13)  <= "0000000000000000000000000000000001" ;
47             memory(14)  <= "0000000000000000000000000000000100" ;
48
49         else
50             if FALLING_EDGE(CLK) then
51                 if MEM_WRITE = '1' then
52                     MEMORY(ADDR_int) <= INPUT;
53                 end if;
54             end if;
55         end if;
56
57     end process;
58
59     ADDRover4 <= ADDRESS(31 downto 2) ;
60     ADDR_int <= CONV_INTEGER(ADDRover4);
61     OUTS <= MEMORY(ADDR_int) when MEM_READ = '1' and (ADDR_int < 64) else
62         (others => 'Z') when MEM_READ = '0' ;
63
64     OUTPUT <= OUTS;
65
66 end BEHAVIORAL;
```

Moving on to the next step, we created a package by the name of “MIPSPackage” where we placed all the previous components and also added several signals that will be used later on in the main module called “MIPSCPU”.

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3
4 package MIPSPackage is
5
6     component ALUControlUnit is
7         Port ( FunctionCode : in  STD_LOGIC_VECTOR (5 downto 0);
8               ALUOp        : in  STD_LOGIC_VECTOR (1 downto 0);
9               ALUFuncnt    : out STD_LOGIC_VECTOR (3 downto 0));
10    end component;
11
12
13
14    component ALU is
15
16        Port ( data1      : in  STD_LOGIC_VECTOR (31 downto 0);
17              data2      : in  STD_LOGIC_VECTOR (31 downto 0);
18              aluop       : in  STD_LOGIC_VECTOR (3 downto 0);
19              cin         : in  STD_LOGIC;
20              dataout     : out STD_LOGIC_VECTOR (31 downto 0);
21              cflag       : out STD_LOGIC;
22              zflag       : out STD_LOGIC;
23              oflag       : out STD_LOGIC);
24
25
26    end component;
27
28
29
30    component CPUMux is
31        Port ( Selector : in  STD_LOGIC;
32              i0        : in  STD_LOGIC_VECTOR (31 downto 0);
33              i1        : in  STD_LOGIC_VECTOR (31 downto 0);
34              Output     : out STD_LOGIC_VECTOR (31 downto 0));
35    end component;
36
```



```

38
39 component DATAMEMORY is
40
41     port ( LoadIt      : in STD_LOGIC;
42           INPUT        : in STD_LOGIC_VECTOR (31 downto 0);
43           OUTPUT       : out STD_LOGIC_VECTOR (31 downto 0);
44           MEM_READ     : in STD_LOGIC;
45           MEM_WRITE    : in STD_LOGIC;
46           ADDRESS      : in STD_LOGIC_VECTOR (31 downto 0);
47           CLK          : in STD_LOGIC
48           );
49
50 end component;
51
52
53
54 component INSTRMEMORY is
55
56     port(
57         LoadIt  : in Std_logic ;
58         DATA   : out STD_LOGIC_VECTOR(31 downto 0);
59         ADDRESS : in STD_LOGIC_VECTOR(31 downto 0);
60         CLK     : in STD_LOGIC
61         );
62 end component;
63
64
65 component MainControlUnit is
66
67     Port ( OpCode      : in  STD_LOGIC_VECTOR (5 downto 0);
68           MemRead     : out  STD_LOGIC;
69           MemWrite    : out  STD_LOGIC;
70           RegDst      : out  STD_LOGIC;
71           Branch      : out  STD_LOGIC;
72           MemtoReg     : out  STD_LOGIC;
73           ALUSrc       : out  STD_LOGIC;
74           ALUOp        : out  STD_LOGIC_VECTOR (1 downto 0);
75           Jump         : out  STD_LOGIC;
76           RegWrite     : out  STD_LOGIC);
77
78 end component;
79
80

```

```

80
81
82     component RegisterFile is
83         Port ( read_sel1  : in  STD_LOGIC_VECTOR (4 downto 0);
84               read_sel2  : in  STD_LOGIC_VECTOR (4 downto 0);
85               write_sel   : in  STD_LOGIC_VECTOR (4 downto 0);
86               write_ena   : in  STD_LOGIC;
87               clk         : in  STD_LOGIC;
88               write_data  : in  STD_LOGIC_VECTOR (31 downto 0);
89               data1       : out STD_LOGIC_VECTOR (31 downto 0);
90               data2       : out STD_LOGIC_VECTOR (31 downto 0));
91     end component;
92
93
94
95     component ShiftLeft2 is
96         Port ( Input  : in  STD_LOGIC_VECTOR (31 downto 0);
97               Output : out STD_LOGIC_VECTOR (31 downto 0));
98     end component;
99
100
101
102     component SignExtend is
103         Port ( Input  : in  STD_LOGIC_VECTOR (15 downto 0);
104               Output : out STD_LOGIC_VECTOR (31 downto 0));
105     end component;
106
107     component PC is
108         Port(
109             signal CLK, RESET : in std_logic;
110             signal Address : in std_logic_vector(31 downto 0);
111             signal PC : out std_logic_vector(31 downto 0)
112         );
113     end component;
114
115     component Adder4 is
116         Port ( Input  : in  STD_LOGIC_VECTOR (31 downto 0);
117               Output : out STD_LOGIC_VECTOR (31 downto 0));
118     end component;
119
120     component JumpAddressConcat is
121         Port ( InputLeft  : in  STD_LOGIC_VECTOR (31 downto 0);
122               InputRight  : in  STD_LOGIC_VECTOR (31 downto 0);
123               Output      : out STD_LOGIC_VECTOR (31 downto 0));
124     end component;
125

```

```

125
126     component Mux5x1 is
127         Port ( S      : in   STD_LOGIC;
128               i0      : in   STD_LOGIC_VECTOR (4 downto 0);
129               i1      : in   STD_LOGIC_VECTOR (4 downto 0);
130               output   : out  STD_LOGIC_VECTOR (4 downto 0));
131     end component;
132 -----start signals-----
133
134 --previous instruction address in PC
135 signal instructionAddress : std_logic_vector(31 downto 0) := X"00000000";
136 signal InstrAddressAdd4   : std_logic_vector(31 downto 0) := X"00000000";
137
138 --related to jump process
139 signal instructionShifted : std_logic_vector(31 downto 0) := X"00000000";
140 signal jumpInstrAddress   : std_logic_vector(31 downto 0) := X"00000000";
141
142 --related to branch process
143 signal branchInstAddress  : std_logic_vector(31 downto 0) := X"00000000";
144 signal immedValue16       : std_logic_vector(31 downto 0) := X"00000000";
145 signal branchValueShifted : std_logic_vector(31 downto 0) := X"00000000";
146 signal intermediateAddress : std_logic_vector(31 downto 0) := X"00000000";
147
148 --final new instruction address result
149 signal newInstrAddress    : std_logic_vector(31 downto 0) := X"00000000";
150
151 --instruction from INSTMEMORY
152 signal instruction        : std_logic_vector(31 downto 0) := X"00000000";
153
154 -----Main control unit signals-----
155 signal MemRead           : std_logic := '0';
156 signal MemWrite          : std_logic := '0';
157 signal RegDst            : std_logic := '0';
158 signal Branch            : std_logic := '0';
159 signal MemtoReg          : std_logic := '0';
160 signal ALUSrc            : std_logic := '0';
161 signal ALUOp             : std_logic_vector(1 downto 0) := "00";
162 signal Jump              : std_logic := '0';
163 signal RegWrite          : std_logic := '0';
164
165 -----Register unit signals-----
166 signal WriteRegister     : std_logic_vector(4 downto 0) := "00000";
167 signal WriteData         : std_logic_vector(31 downto 0) := X"00000000";
168 signal ReadData1        : std_logic_vector(31 downto 0) := X"00000000";
169 signal ReadData2        : std_logic_vector(31 downto 0) := X"00000000";
170

```

```

165 -----Register unit signals-----
166 signal WriteRegister      : std_logic_vector(4 downto 0) := "00000";
167 signal WriteData          : std_logic_vector(31 downto 0) := X"00000000";
168 signal ReadData1          : std_logic_vector(31 downto 0) := X"00000000";
169 signal ReadData2          : std_logic_vector(31 downto 0) := X"00000000";
170
171 -----ALU unit & control signals-----
172 signal ALUFuncnt          : std_logic_vector(3 downto 0)  := "0000";
173 signal ALUZero            : std_logic := '0';
174 signal ALUMuxInput        : std_logic_vector(31 downto 0) := X"00000000";
175 signal ALUOutTemp         : std_logic_vector(31 downto 0) := X"00000000";
176
177 -----Data Memory signals-----
178 signal DataMemOutTemp     : std_logic_vector(31 downto 0) := X"00000000";
179
180
181
182
183 --open signal for later adding
184
185 signal BranchingSignal : std_logic := '0';
186
187
188 -----end signals-----
189
190 end MIPSPackage;
191
192 package body MIPSPackage is
193 end MIPSPackage;
194

```

Coming to the final stage, we created a main module named “MIPSCPU” and included the “MIPSPackage” where the main module will be completed by making all the connections between all the previous modules according to the connections drawn in diagram of the CPU provided in the major task pdf.

At the beginning, we declared all the inputs and outputs exactly as mentioned in the major task pdf and as can be seen in the upcoming screenshot, however, we decided to add two extra outputs “ReadReg1O” and “ReadReg2O” to display the address of the registers that are used in the reading process in the current instruction in order to ease the output tracing at the end in the simulation.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use work.MIPSPackage.all;
4
5  entity MIPSCPU is
6      Port ( START      : in  STD_LOGIC;
7            CLK         : in  STD_LOGIC;
8            RegFileOut1 : out STD_LOGIC_VECTOR (31 downto 0);
9            RegFileOut2 : out STD_LOGIC_VECTOR (31 downto 0);
10           ALUOut       : out STD_LOGIC_VECTOR (31 downto 0);
11           PCOut        : out STD_LOGIC_VECTOR (31 downto 0);
12           DataMemOut   : out STD_LOGIC_VECTOR (31 downto 0);
13
14           -----The previous outputs are the ones requ
15           --The next outputs are added as extras by us to verify that the f
16
17           ReadReg1O    : out STD_LOGIC_VECTOR (4 downto 0);
18           ReadReg2O    : out STD_LOGIC_VECTOR (4 downto 0)
19           );
20 end MIPSCPU;
21
```

Next, we used the previously created signals and components found in “MIPSPackage” to make the connections between the modules like the diagram of the CPU given in the major task pdf with just a small modification for adding the “bne” instruction. So we wrote the port maps using the created signals when needed and any output that is found in one of the components but wont be used in the main module was assigned to “open”. At the end, we assigned the outputs of the main module called “MIPSCPU” to their equivalent signals.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use work.MIPSPackage.all;
4
5  entity MIPSCPU is
6      Port ( START      : in  STD_LOGIC;
7            CLK         : in  STD_LOGIC;
8            RegFileOut1 : out STD_LOGIC_VECTOR (31 downto 0);
9            RegFileOut2 : out STD_LOGIC_VECTOR (31 downto 0);
10           ALUOut       : out STD_LOGIC_VECTOR (31 downto 0);
11           PCOut        : out STD_LOGIC_VECTOR (31 downto 0);
12           DataMemOut   : out STD_LOGIC_VECTOR (31 downto 0);
13
14           -----The previous outputs are the ones requested in the Major Task PDF-----
15           --The next outputs are added as extras by us to verify that the fibonnaci sequence appears in $s0 whose decimal value is 16--
16
17           ReadReg10    : out STD_LOGIC_VECTOR (4 downto 0);
18           ReadReg20    : out STD_LOGIC_VECTOR (4 downto 0);
19       );
20 end MIPSCPU;
21
22 architecture Behavioral of MIPSCPU is
23     -----Signals used in this module is found in the package-----
24 begin
25
26
27
28     -----PC related operations-----
29     PC_Adder      : Adder4          port map (Input => instructionAddress, Output => InstrAddressAdd4);
30
31     --Branch related
32     Branch_PC_Sign : SignExtend     port map (Input => instruction(15 downto 0), Output => immedValue16);
33     Branch_PC_Shift : ShiftLeft2    port map (Input => immedValue16, Output => branchValueShifted);
34     Branch_PC_Adder : ALU           port map (data1 => InstrAddressAdd4, data2 => branchValueShifted, aluop => "0010", cin => '0'
35                                             , dataout => branchInstAddress, cflag => open, zflag =>open, oflag =>open);
36     BranchingSignal <= Branch AND ((ALUZero AND NOT(instruction(26))) OR (NOT(ALUZero) AND instruction(26)));
37     PC_BranchMux   : CPUMux         port map (Selector => BranchingSignal, i0 => InstrAddressAdd4, i1 => branchInstAddress
38                                             , Output => intermediateAddress);
39
40     --Jump related
41     PC_Shifter     : ShiftLeft2     port map (Input => instruction, Output => instructionShifted);
42     PC_JumpConc    : JumpAddressConcat port map (InputLeft => InstrAddressAdd4, InputRight => instructionShifted
43                                             , Output => jumpInstrAddress);
44     PC_JumpMux     : CPUMux         port map (Selector => Jump, i0 => intermediateAddress, i1 => jumpInstrAddress
45                                             , Output => newInstrAddress);
46
47     --PC final impact
48     Program_Counter : PC           port map (CLK => CLK, RESET => START , Address => newInstrAddress, PC => instructionAddress);
49
50


```

```


48
49
50 -----Instruction memory unit-----
51
52 Instr_Memory      : INSTRMEMORY      port map (LoadIt => START, DATA => instruction, ADDRESS => instructionAddress, CLK => CLK);
53
54
55 -----Main Control Unit-----
56
57 Control_Unit      : MainControlUnit    port map (OpCode => instruction(31 downto 26), MemRead => MemRead, MemWrite => MemWrite
58 , RegDst => RegDst, Branch => Branch, MemtoReg => MemtoReg, ALUSrc => ALUSrc
59 , ALUOp => ALUOp, Jump => Jump, RegWrite => RegWrite);
60
61 -----Registers unit-----
62 CPU_WriteRegMUX    : Mux5x1            port map (S => RegDst, i0 => instruction(20 downto 16), i1 => instruction(15 downto 11)
63 , output => WriteRegister);
64
65 CPU_Registers      : RegisterFile       port map (read_sel1 => instruction(25 downto 21), read_sel2 => instruction(20 downto 16)
66 , write_sel => WriteRegister, write_ena => RegWrite, clk => CLK
67 , write_data => WriteData, data1 => ReadData1, data2 => ReadData2);
68
69 -----ALU & ALU Control unit-----
70
71 ALU_Control        : ALUControlUnit     port map (FunctionCode => instruction(5 downto 0), ALUOp => ALUOp, ALUFunct => ALUFunct);
72
73 ALU_InputMux       : CPUMux             port map (Selector => ALUSrc, i0 => ReadData2, i1 => immedValue16
74 , Output => ALUMuxInput);
75
76 ALU_Unit           : ALU                port map (data1 => ReadData1, data2 => ALUMuxInput, aluop => ALUFunct, cin => '0'
77 , dataout => ALUOutTemp, cflag => open, zflag => ALUZero, oflag => open );
78 -----Data memory unit-----
79
80 Data_Memory        : DATAMEMORY         port map (LoadIt => START, INPUT => ReadData2, OUTPUT => DataMemOutTemp
81 , MEM_READ => MemRead, MEM_WRITE => MemWrite, ADDRESS => ALUOutTemp, CLK => CLK);
82 Data_MemMuxOut     : CPUMux             port map (Selector => MemtoReg, i0 => ALUOutTemp, i1 => DataMemOutTemp
83 , Output => WriteData);
84
85 -----Outputs-----
86 RegFileOut1 <= ReadData1;
87 RegFileOut2 <= ReadData2;
88 ALUOut        <= ALUOutTemp;
89 PCOut         <= instructionAddress;
90 DataMemOut    <= DataMemOutTemp;
91 ReadReg10 <= instruction(25 downto 21);
92 ReadReg20 <= instruction(20 downto 16);
93
94 end Behavioral;

```

## The MIPS CPU RTL Schematic

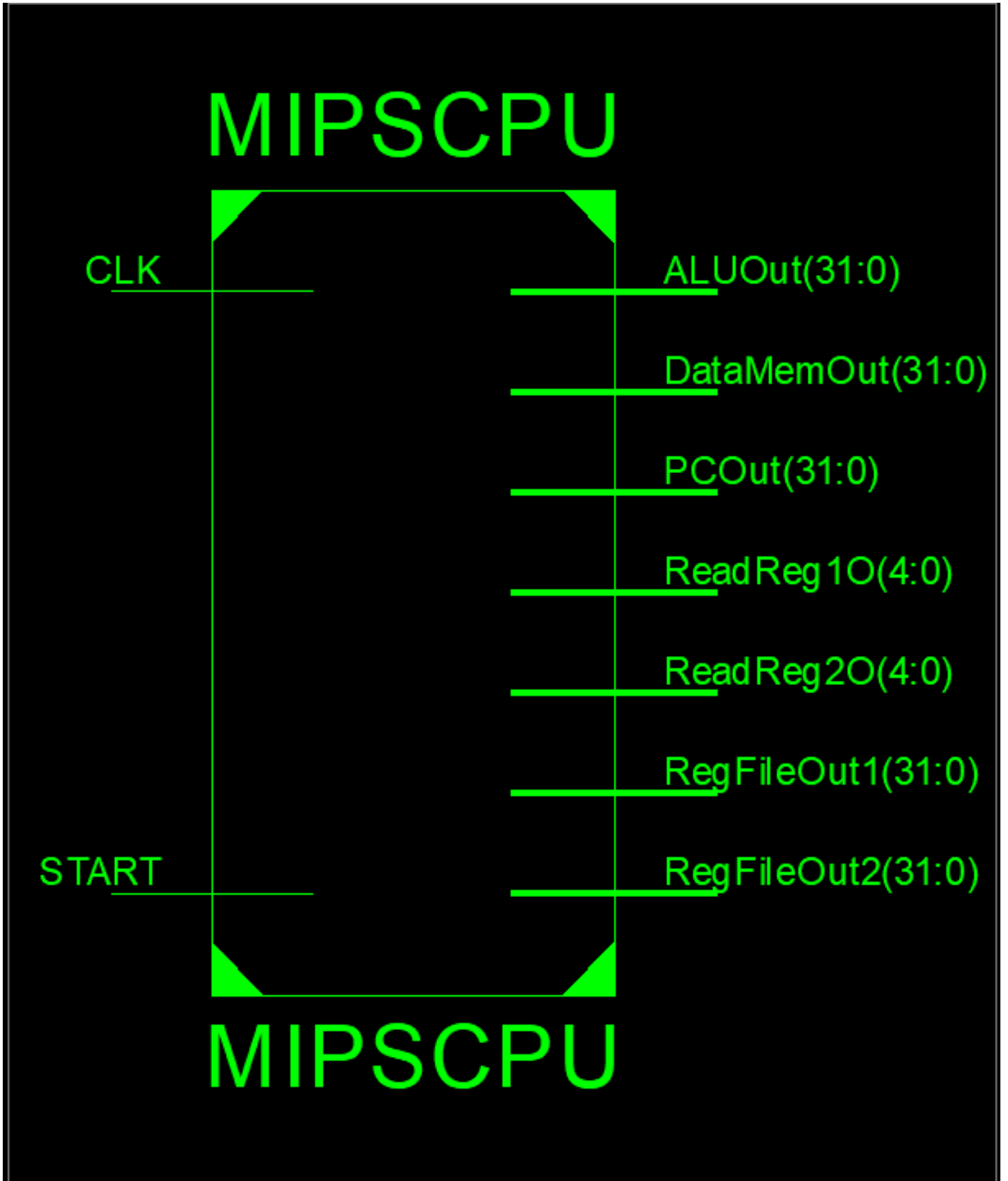



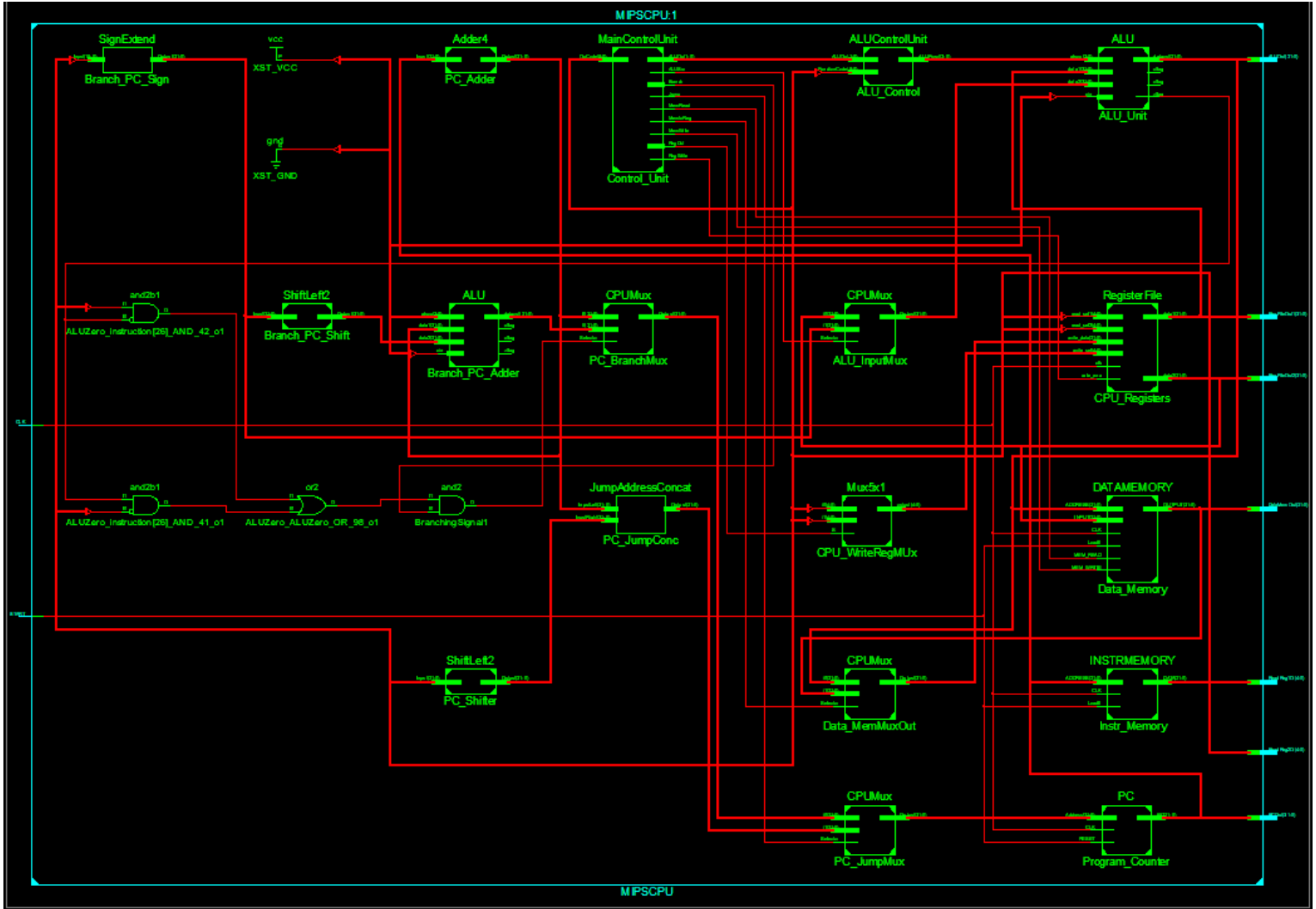

## The MIPS CPU Testbench Code

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4
5  ENTITY test_instr IS
6  END test_instr;
7
8  ARCHITECTURE behavior OF test_instr IS
9
10     -- Component Declaration for the Unit Under Test (UUT)
11
12     COMPONENT MIPSCPU
13     PORT (
14         START : IN  std_logic;
15         CLK : IN  std_logic;
16         RegFileOut1 : OUT  std_logic_vector(31 downto 0);
17         RegFileOut2 : OUT  std_logic_vector(31 downto 0);
18         ALUOut : OUT  std_logic_vector(31 downto 0);
19         PCOut : OUT  std_logic_vector(31 downto 0);
20         DataMemOut : OUT  std_logic_vector(31 downto 0);
21         ReadReg10 : out STD_LOGIC_VECTOR (4 downto 0);
22         ReadReg20 : out STD_LOGIC_VECTOR (4 downto 0)
23     );
24     END COMPONENT;
25
26
27
28     --Inputs
29     signal START : std_logic := '0';
30     signal CLK : std_logic := '0';
31
32     --Outputs
33     signal RegFileOut1 : std_logic_vector(31 downto 0);
34     signal RegFileOut2 : std_logic_vector(31 downto 0);
35     signal ALUOut : std_logic_vector(31 downto 0);
36     signal PCOut : std_logic_vector(31 downto 0);
37     signal DataMemOut : std_logic_vector(31 downto 0);
38     signal ReadReg10 : std_logic_vector(4 downto 0);
39     signal ReadReg20 : std_logic_vector(4 downto 0);
40
41
42     -- Clock period definitions
43     constant CLK_period : time := 10 ns;
```


```

44
45 BEGIN
46
47     -- Instantiate the Unit Under Test (UUT)
48     uut: MIPSCPU PORT MAP (
49         START => START,
50         CLK => CLK,
51         RegFileOut1 => RegFileOut1,
52         RegFileOut2 => RegFileOut2,
53         ALUOut => ALUOut,
54         PCOut => PCOut,
55         DataMemOut => DataMemOut,
56         ReadReg10 => ReadReg10,
57         ReadReg20 => ReadReg20
58
59
60
61         );
62
63     -- Clock process definitions
64     CLK_process :process
65     begin
66         CLK <= '0';
67         wait for CLK_period/2;
68         CLK <= '1';
69         wait for CLK_period/2;
70     end process;
71
72
73     -- Stimulus process
74     stim_proc: process
75     begin
76
77         START <= '1';
78         WAIT for 30 ns;
79         START <= '0';
80         WAIT for 30ns;
81
82
83         wait;
84     end process;
85
86 END;
87

```
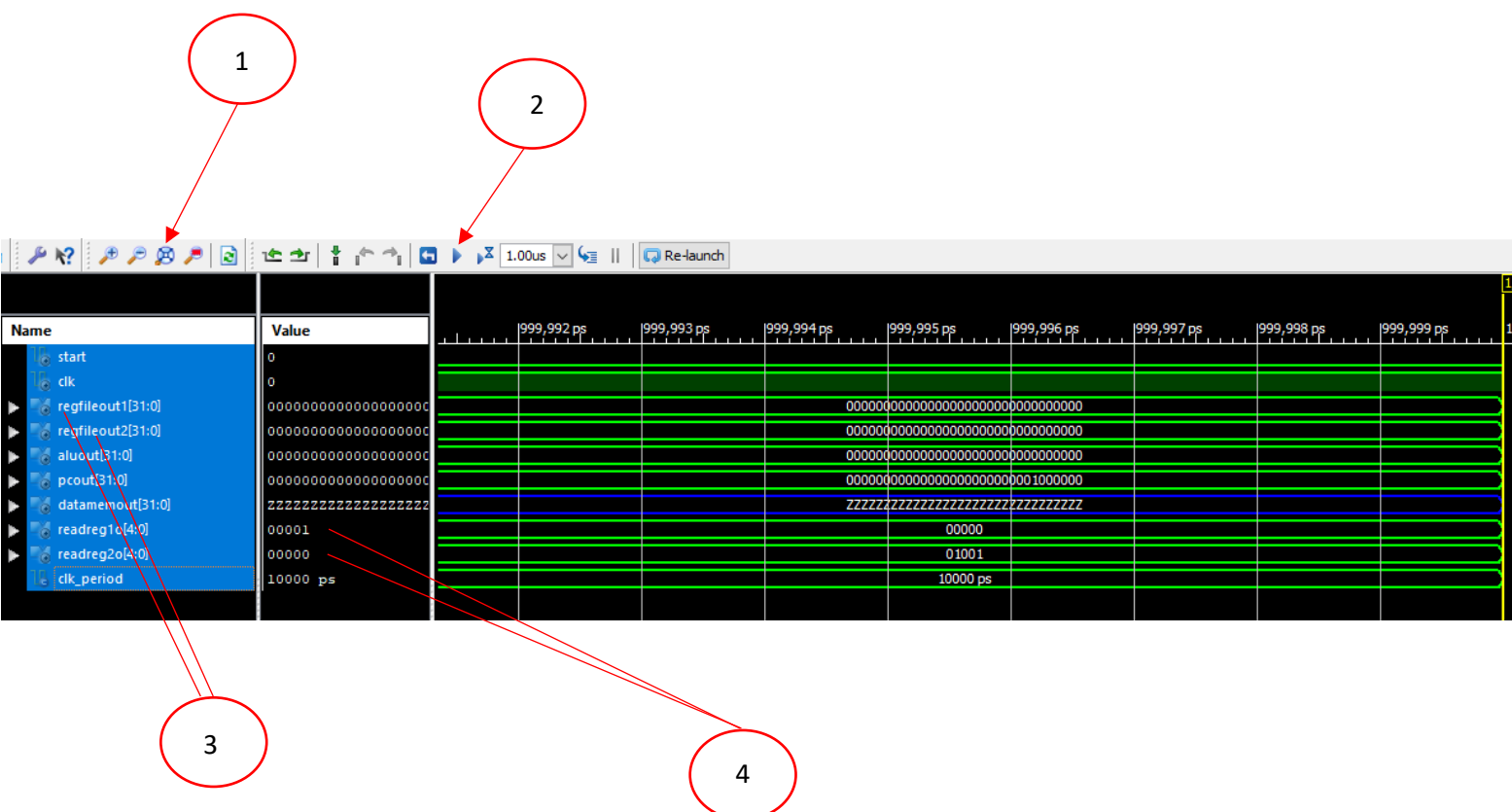
## The MIPS CPU Sample Output

At the beginning of the simulation, a few steps should be done in order to see the output and making the tracing process easier. Step 1 is to fit the page to the screen. Step 2 is to press the “Run All” button in order to display all the program including the output because by default it stops at 1000 ns which is not sufficient. Step 3 is to change the radix of “regfileout1” and “regfileout2” to signed decimal in order to read the Fibonacci sequence in decimals which is easier. Step 4 is to change the radix of the two extra outputs of “readreg1o” and “readreg2o” to unsigned decimal to display the address of the registers in use (the address of the registers does not use the sign) to trace the outputs of the required register \$s0 by checking the values in the registers output when either of the “readreg1o” or “readreg2o” is equal to “16” which is the decimal number of “10000” which is the address of \$s0 in MIPS.



For approximately the first 1100 – 1150 ns, this was the time related to the first instructions of calculating actually the values and the other needed instructions, but from nearly the 1150 ns till the end, this was the time of the loop outputting the sequence of Fibonacci. Accordingly, the output of the sequence could be seen starting from nearly 1150 ns.

[illegible]

At 1153.272 ns, the program started in executing the loop related to outputting the Fibonacci sequence. As it can be seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had ‘1’ as its output which is the first number in the Fibonacci sequence.

[illegible]

Proceeding forward with 70 more nanoseconds, at 1223.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had ‘1’ as its output which is the second number in the Fibonacci sequence.

[illegible]

Proceeding forward with 70 more nanoseconds, at 1293.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had ‘2’ as its output which is the third number in the Fibonacci sequence.

[illegible]

Proceeding forward with 70 more nanoseconds, at 1363.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had ‘3’ as its output which is the fourth number in the Fibonacci sequence.

[illegible]

Proceeding forward with 70 more nanoseconds, at 1433.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had ‘5’ as its output which is the fifth number in the Fibonacci sequence.

[illegible]

Proceeding forward with 70 more nanoseconds, at 1503.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had ‘8’ as its output which is the sixth number in the Fibonacci sequence.

[illegible]

Proceeding forward with 70 more nanoseconds, at 1573.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had “13” as its output which is the seventh number in the Fibonacci sequence.



[illegible]

Proceeding forward with 70 more nanoseconds, at 1643.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had “21” as its output which is the eighth number in the Fibonacci sequence.

[illegible]


Proceeding forward with 70 more nanoseconds, at 1713.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had “34” as its output which is the ninth number in the Fibonacci sequence.

[illegible]


Proceeding forward with 70 more nanoseconds, at 1783.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had “55” as its output which is the tenth number in the Fibonacci sequence.

[illegible]

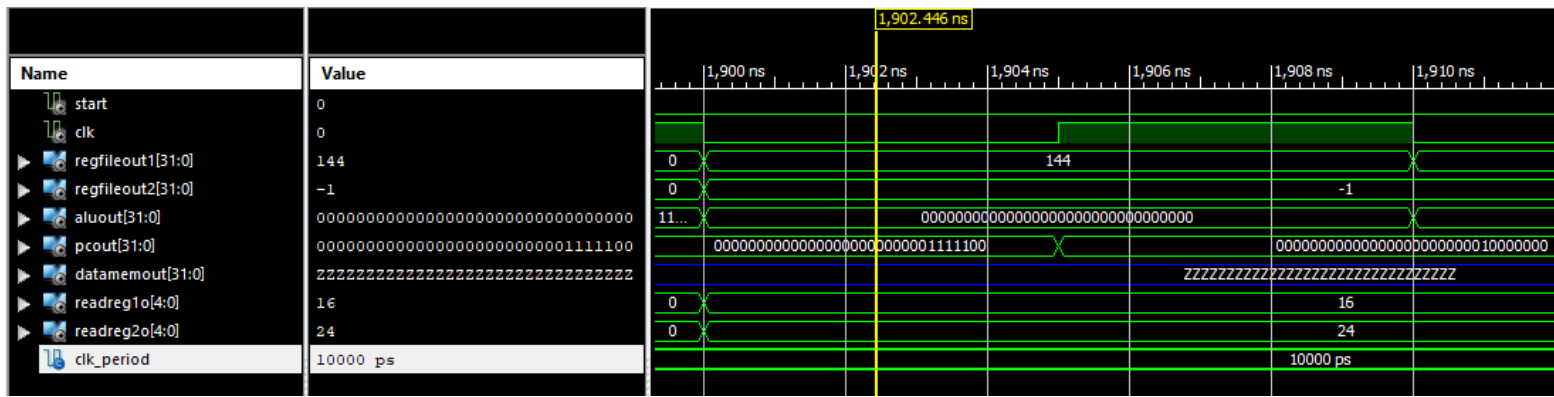Proceeding forward with 70 more nanoseconds, at 1853.272 ns and as seen, when “readreg2o” is equal to “16” which is the address of register \$s0, “regfileout2” had “89” as its output which is the eleventh number in the Fibonacci sequence.



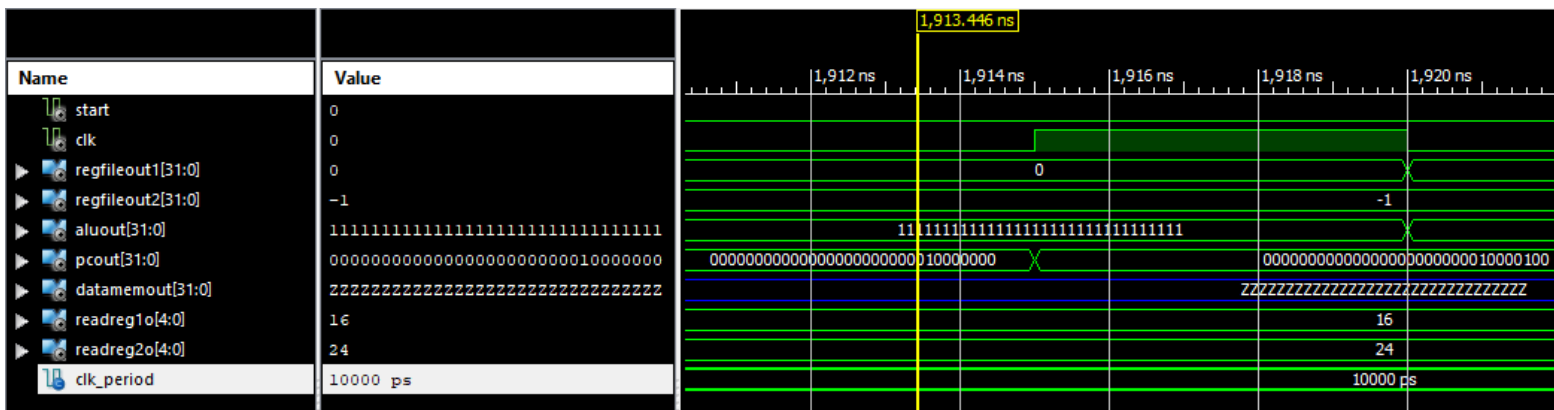Then at 1902.446 ns and as seen, when “readreg1o” is equal to “16” which is the address of register \$s0, “regfileout1” had “144” as its output which is the twelfth number in the Fibonacci sequence.



Then at 1913.446 ns and as seen, when “readreg1o” is equal to “16” which is the address of register \$s0, “regfileout1” had ‘0’ as its output which is the required number to appear after displaying the first twelve Fibonacci numbers.

[illegible]

Then at 1921.839 ns and as seen, when “readreg1o” is equal to “16” which is the address of register \$s0, “regfileout1” had ‘-1’ as its output which is the final number required to appear in the output.

## **Team Members'**

### **Equivalent Contribution**

- Ahmed Hossam Moussa Sakr (20P1009) – Wrote the codes of: “ALUControlUnit”, “CPUMux” and half the code of the “MainControlUnit” modules with overall contribution of 20% of the total effort.
  
- Mohamed Tarek Mohamed Abdalla Ahmed Khafagy (20P6211) – Wrote the codes of: “ShiftLeft2”, “RegisterFile” and “TheDecoder” modules with overall contribution of 20% of the total effort.
  
- Ahmed Wael Samir Abdelmegied (20P7271) – Wrote the codes of: “ALU”, “SignExtend” and “JumpAddressConcat” with overall contribution of 20% of the total effort.
  
- Omar Ahmed Mohamed Gamaleldin Swelam (21P0405) – Wrote the codes of: “MIPSCPU”, “PC” and half the code of the “MainControlUnit” modules with overall contribution of 20% of the total effort.

- Tamer Ihab Mohamed Abdelwahab 20P5567 – Wrote the codes of: “RegDef”, “Mux32x1”, “Mux5x1” and “Adder4” modules with overall contribution of 20% of the total effort.
- All the members participated in the editing of the “INSTRMEMORY”, test benching the “ALU”, “RegisterFile” and “MIPSCPU”.